
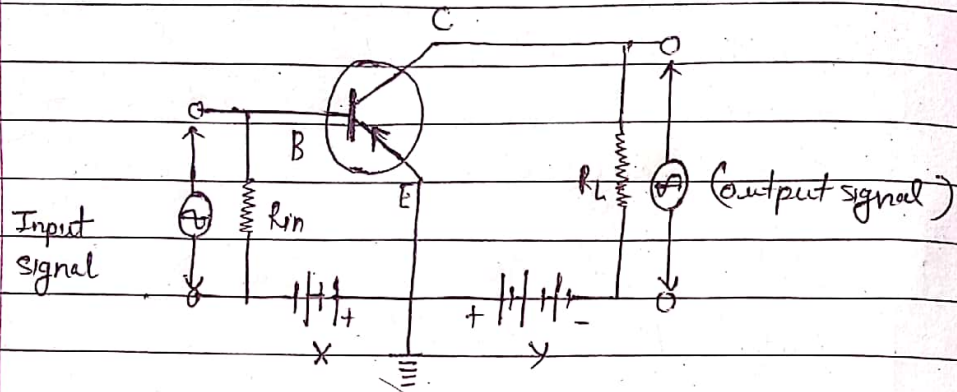


Common Emitter Transistor amplifier.

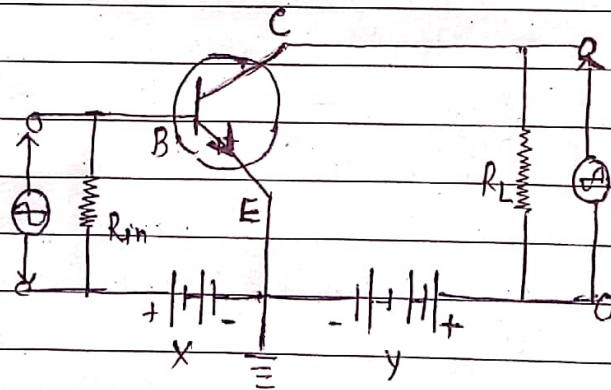Show respectively the PNP and NPN Transistor amplifiers in common emitter configuration



[PNP Transistor]



[NPN - Transistor]

The Input circuit is kept in forward bias by the battery X while the output circuit is kept

Am

in reverse bias by the battery  $V$   
 The Input signal is applied between  
 the terminals of base B and  
 emitter E and the output  
 Voltage is obtained across the load  
 resistance  $R_L$  connected in series with  
 the battery  $V$  in between the collector  
 (C) and emitter (E) terminals

(a) Current gain  $\Rightarrow$  At a constant collector  
 voltage  $V_{CE}$  the  
 ratio of change in collector current  
 to the corresponding change in base  
 current is called the current gain  
 by a common emitter amplifier and  
 It is represented by the symbol  $\beta$   
 thus

$$\text{Current gain } \beta = \left( \frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$$

Its value is generally 40

(b) Voltage gain  $\Rightarrow$

$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{R_L \Delta I_C}{R_{in} \Delta I_B}$$

$$= \frac{R_L}{R_{in}} \times \left( \frac{\Delta I_C}{\Delta I_B} \right)$$

$$= \beta \frac{R_L}{R_{in}}$$

(c) power gain

By definition power gain = Current gain  $\times$  Voltage gain

$$A_p = \beta \times \beta \left( \frac{R_L}{R_{in}} \right)$$

$$= \beta^2 \frac{R_L}{R_{in}}$$

(d) Input Impedance  $R_{in}$  =  $\left( \frac{\Delta V_B}{\Delta I_B} \right)_{V_C}$

Its value is nearby in between

200  $\Omega$  to 800  $\Omega$

(e) output impedance

$$R_{out} = \left( \frac{\Delta V_C}{\Delta I_C} \right)_{I_B}$$

Its value is nearby of the order

of 20 k $\Omega$